

EE133/233 FM Radio Receiver


System Overview — Final Project

Edison Altamirano (006948159) Sahan (006948160)

EE133/233 — Stanford University

March 2026

Full System Architecture

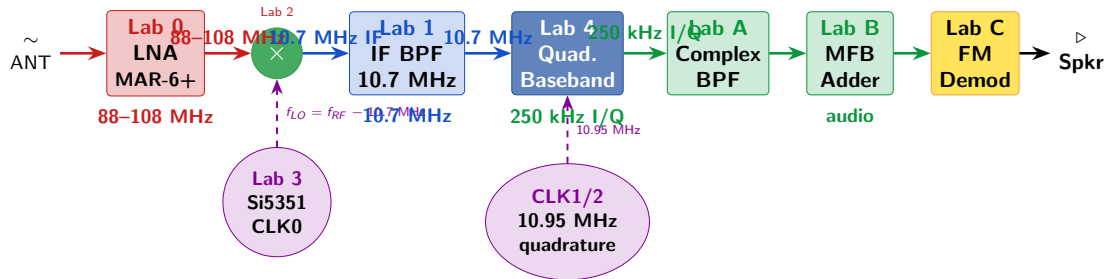

RF Stage

Antenna → LNA → Mixer
88–108 MHz → 10.7 MHz

IF Stage

IF BPF selects 10.7 MHz
Image rejection + channel
filtering

Baseband

I/Q → Complex BPF → FM
demod
250 kHz → audio

Lab 0 — MAR-6+ Low-Noise Amplifier

What it does


The MAR-6+ is the first stage amplifier. It sets the noise floor for the entire receiver (Friis equation):

$$F_{\text{sys}} \approx F_1 + \frac{F_2 - 1}{G_1}$$

With $G_1 \approx 22$ dB, noise from all later stages is suppressed by $\times 158$.

Parameter	Value
IC	MAR-6+ (Mini-Circuits)
Gain	≈ 22 dB @ 100 MHz
NF	2.3 dB
Bandwidth	1 MHz – 1 GHz

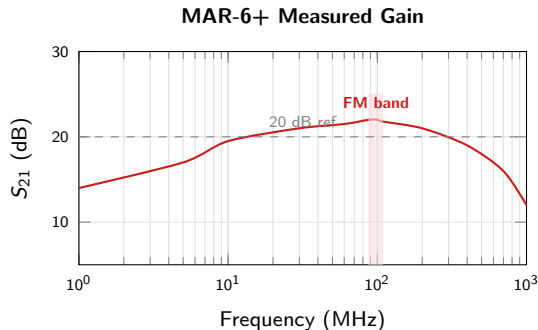
S_{21} gain vs frequency (NanoVNA measurement)



–48 dBm

Lab 2 — ADE-1 Diode Ring Mixer: First Downconversion

Frequency translation

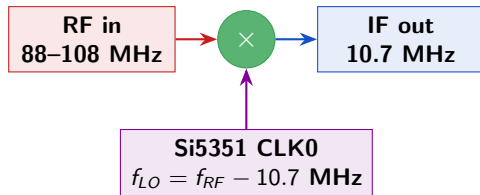


Example (tuned to 98.1 MHz):

$$f_{LO} = 98.1 - 10.7 = \mathbf{87.4 \text{ MHz}}$$

$$f_{IF} = |f_{RF} - f_{LO}| = \mathbf{10.7 \text{ MHz}}$$

Mixer output spectrum (RF = 98.1 MHz)

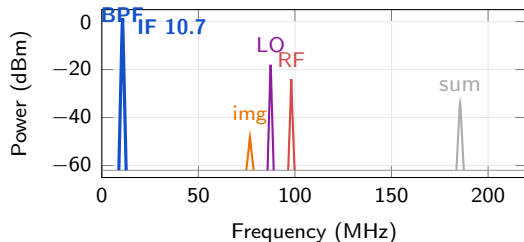

Product	Formula	Value
IF	$ f_{RF} - f_{LO} $	10.7 MHz
Image	$f_{LO} - 10.7$	76.7 MHz
LO leak	f_{LO}	87.4 MHz
Sum	$f_{RF} + f_{LO}$	185.5 MHz

Lab 3 — Si5351 LO: Quadrature Generation

Silicon Labs Si5351 Fractional-N PLL

- Programmable PLL controlled via I²C
- Controlled by **Raspberry Pi Pico 2W** over WiFi HTTP
- **CLK0**: first LO for Lab 2 mixer
 $f_{CLK0} = f_{RF} - 10.7 \text{ MHz}$
Covers 77.3–97.3 MHz (full FM band)
- **CLK1/CLK2**: quadrature LO at 10.95 MHz
90° offset via `set_phase(CLK2, 64)`
VCO runs at $64 \times f_{out}$ on PLLA

Quadrature clock generation (Pico 2W firmware):

```
// CLK1 = 0°, CLK2 = 90° (both on PLLA)
si5351.set_freq(quad_hz * RATIO, PLLA, CLK1);
si5351.set_freq(quad_hz * RATIO, PLLA, CLK2);

si5351.set_phase(CLK1, 0); // 0°
si5351.set_phase(CLK2, 64); // 90°
si5351.pll_reset(PLLA); // lock phase
```

Lab 3 — Station Tuning and Phase Control

Station tuning via HTTP API:

```
// First LO --- tune to FM station X:  
GET /api/clk2/set?mhz=X  
CLK0 = X - 10.700 MHz  
  
// Quadrature LO --- fixed at 10.95 MHz:  
GET /api/quad/set?mhz=10.95
```

Why phase matters:

- `pll_reset(PLLA)` enforces coherent start
- $\text{RATIO} = 64 \Rightarrow \text{VCO at } 64 \times 10.95 = 700.8 \text{ MHz}$
- One VCO cycle = $\frac{1}{700.8 \text{ MHz}}$; 64 cycles = $\frac{1}{10.95 \text{ MHz}} = \text{one full period} \Rightarrow$
exactly 90°

Lab 1 — 10.7 MHz IF BPF & Impedance Matching

The problem

Ceramic BPF impedance $Z_0 \approx 330 \Omega$ vs system 50Ω .

Without matching:

- VSWR = 6.8 $S_{21} \approx -20$ dB
- Most power reflected; signal lost


L-network solution ($50 \rightarrow 330 \Omega$):

$$L_s = 1.76 \mu\text{H}, \quad C_p = 106.7 \text{ pF}, \quad Q_T = 2.37$$

With matching:

- VSWR ≈ 1.05 $S_{21} \approx -4.5$ dB
- 15.5 dB improvement

S_{21} : matched vs unmatched

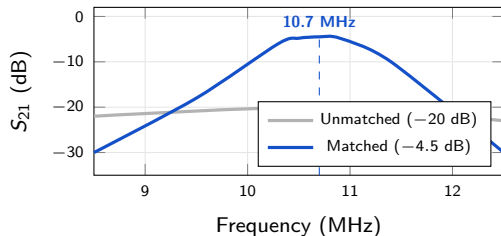


Lab 4 — Quadrature I/Q Downconversion

Three cascaded boards:

- 1 **ADT1-4W** transformer: 1:4 impedance, SE $\rightarrow$ differential
- 2 **74CBTLV3253**: quadrature analog switches
Driven at $0^\circ/90^\circ/180^\circ/270^\circ$ by Si5351 CLK1/CLK2
- 3 **AD4940-1** FDA: dual LPF + gain = 2

Note: 74ALVC74 ($\div 4$) not used. Si5351 provides quadrature directly via `set_phase(CLK2, 64)`.

I/Q phasor view

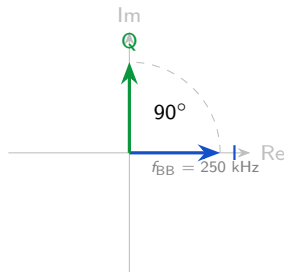

Lab 4 — Quadrature I/Q Downconversion

Frequency math:

$$f_{\text{quad}} = 10.95 \text{ MHz}$$


$$f_{\text{low-IF}} = |f_{\text{IF}} - f_{\text{quad}}| = |10.70 - 10.95| = \mathbf{250 \text{ kHz}}$$

Measured result:

I and Q outputs both show tone at 250 kHz.

C1: $5.45 \text{ V}_{\text{pk-pk}}$, C2: $5.46 \text{ V}_{\text{pk-pk}} \Rightarrow$ balanced amplitudes confirm 90° phase relationship.

Spectrum at baseband:

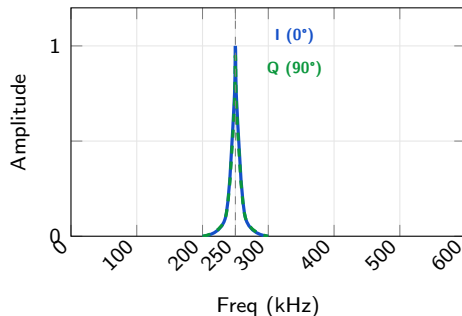


Experiment 1 — Quadrature + LPF: Hardware Validation

Setup: ADT1-4W + 74CBTLV3253 + AD4940-1 LPF (no complex BPF)

IF = 10.7 MHz $f_{\text{quad}} = 10.95 \text{ MHz} \Rightarrow \text{low-IF} = 250 \text{ kHz}$

Oscilloscope (I/Q waveforms)

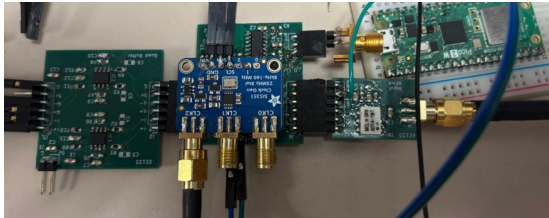

C1 (orange) = I channel C2 (blue) = Q channel
Both at 250 kHz, balanced amplitudes ≈ 5.45
 $V_{\text{pk-pk}}$

Spectrogram (Digilent WaveForms)





Tone at 250 kHz clearly visible in both channels.

Both I and Q pass the desired tone — image rejection not yet applied.

Lab A — Complex BPF: Simulation Results

Single-path measurement (polyproc.m, esI/esQ)

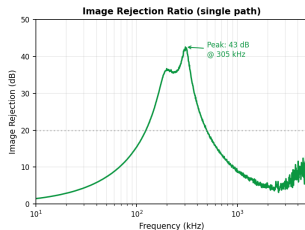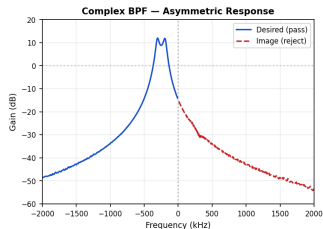Asymmetric response: desired pass vs image reject, + image rejection ratio:




Lab A — Cross-coupled Tow-Thomas (4× THS4551)

- Cross-coupled I/Q paths $\Rightarrow$ **asymmetric** frequency response
- Passes -300 kHz sideband (desired)
- Rejects $+300$ kHz sideband (image)
- Single path: $\approx$ **43** dB rejection

Lab B — MFB Adder: Simulation Results

Full chain (ActProcB.m, espl/Q + esml/Q)

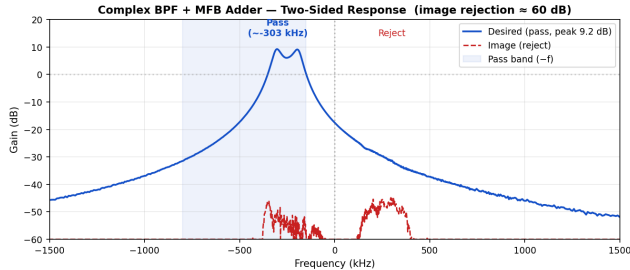Complex BPF + MFB adder two-sided response:



Lab B — MFB Adder ($1 \times$ THS4551)

- Combines $I' + Q'$ into one real differential signal
- Full chain rejection: ≈ 60 dB at 303 kHz
- Output feeds Lab C FM demodulator


Path	Image Rej.
Single path	≈ 43 dB
Full chain	≈ 60 dB

Experiment 2 — Quad + Complex BPF + Adder: Hardware Validation

Setup: Exp. 1 chain + Complex BPF (Tow-Thomas, 250 kHz) + MFB Adder

Expected: desired tone passes, image tone **suppressed by ≈ 60 dB**

Oscilloscope (after Complex BPF + Adder)

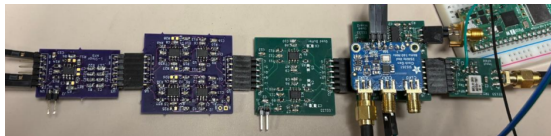

C1 (orange): tone at 250 kHz (desired) — present
C2 (blue): image sideband — **strongly suppressed**

Desired tone at 250 kHz retained.

Image component greatly attenuated — confirms
 ≈ 60 dB rejection.

Spectrogram (after Complex BPF + Adder)



Compared to Exp. 1: C2 now shows image suppression instead of equal amplitude.

Lab C — FM Demodulation Board

Lab C — FM Demodulation Board

- Inputs: In+, In−, VDD, GND (differential)
- FM discriminator: Δf deviation $\rightarrow$ voltage
- Audio band recovered: 20 Hz – 15 kHz $\rightarrow$ Speaker

Key measurements:


- **LNA:** +22 dB gain, 2.3 dB NF (FM band, flat)
- **IF BPF:** +15.5 dB after L-network matching
- **Quadrature:** 250 kHz low-IF, balanced I/Q confirmed
- **Complex BPF:** $\approx$ 60 dB image rejection
- **Audio:** recovered at speaker ✓

Conclusion — End-to-End FM Receiver

One station's journey (98.1 MHz):

Stage	In	Out
Lab 0 LNA	-70 dBm RF	-48 dBm RF
Lab 2 Mixer	98.1 + 87.4 MHz	10.7 MHz IF
Lab 1 BPF	mixed products	10.7 MHz clean
Lab 4 I/Q	10.7 MHz IF	250 kHz I/Q
Lab A CBF	± 250 kHz	-250 kHz only
Lab B Adder	I', Q'	combined real
Lab C Demod	FM signal	audio

Gain budget across chain:

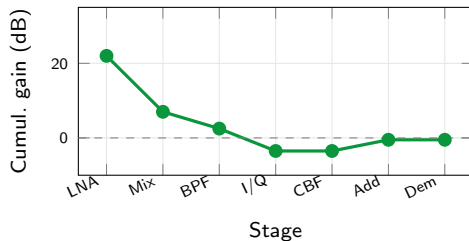

Antenna → Speaker

88–108 MHz → 10.7 MHz → 250 kHz →
audio